



NGSPICE Tutorial


By
Yogesh Mahajan and
Shashank OV

Bridge Courses, IIT Bombay (July, 2018)




What is NGSPICE ?

- ❑ Spice is an acronym for the **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis. First developed by UC Berkeley. It is the origin of most modern circuit simulators.
- ❑ NGSPICE is an open source mixed signal/mixed level simulator. It is the result of combining SPICE with some extra analysis, modeling methods and device simulation features.
- ❑ It is available for Linux, MAC and Windows. *It is recommended to use Linux system for NGSPICE.*
- ❑ NGSPICE requires a circuit described in netlist format. A *netlist* is defined as a set of circuit components and their interconnection. It may also include simulation controls.

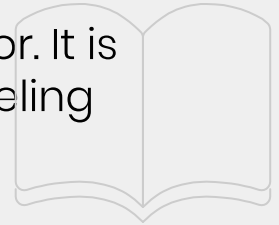

NGSPICE provides you with ...

- Basic circuit elements
 - Passive components: resistors, capacitors, inductors, etc.
 - Sources: voltage and current sources, controlled sources
- Semiconductor devices
 - Pre-defined circuit elements such as diodes, BJTs, MOSFETs, etc.
 - Allows user to add device specific models for more complicated devices such as OpAmps and specialized transistors (technology dependent models)
- Circuit analysis techniques
 - DC, AC (small signal) analysis
 - Transient analysis
 - Noise, Pole-Zero analysis and more
- Plot, save and measure analysis results

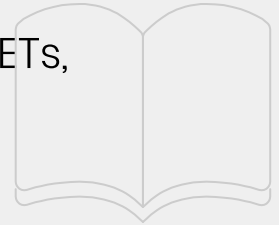

Getting started with NGSPICE

```
1  Resistive Divider Circuit
2
3  * Resistors
4  R2 out gnd 10k
5  R1 in out 10k
6  * Voltage Source
7  v1 in gnd dc 1V
8
9  * Control block starts here
10 .control
11 dc v1 0 10 0.1
12 * print v(out) v(in)
13 plot v(out) v(in)
14 plot i(v1)
15 .endc
16
17 .end
18
```

Title

Circuit Elements

Analysis and Plot

End of File


Common Circuit Elements

First letter	Element description
C	Capacitor
D	Diode
F	Current-controlled current source (CCCs)
G	Voltage-controlled current source (VCCS)
I	Current source
J	Junction field effect transistor (JFET)
L	Inductor
M	Metal oxide field effect transistor (MOSFET)
Q	Bipolar junction transistor (BJT)
R	Resistor
X	Subcircuit (for details see below)
Z	Metal semiconductor field effect transistor (MESFET)


Scaling Factors


Suffix	Name	Factor
T	Tera	10^{12}
G	Giga	10^9
Meg	Mega	10^6
K	Kilo	10^3
mil	Mil	25.4×10^{-6}
m	milli	10^{-3}
u	micro	10^{-6}
n	nano	10^{-9}
p	pico	10^{-12}
f	femto	10^{-15}

**Let's start
with a
simple
circuit**

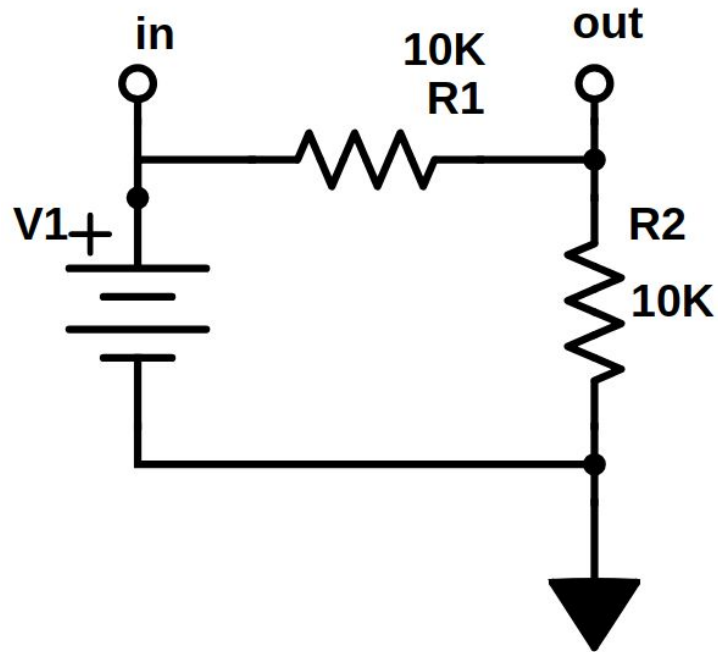

Schmitt Trigger

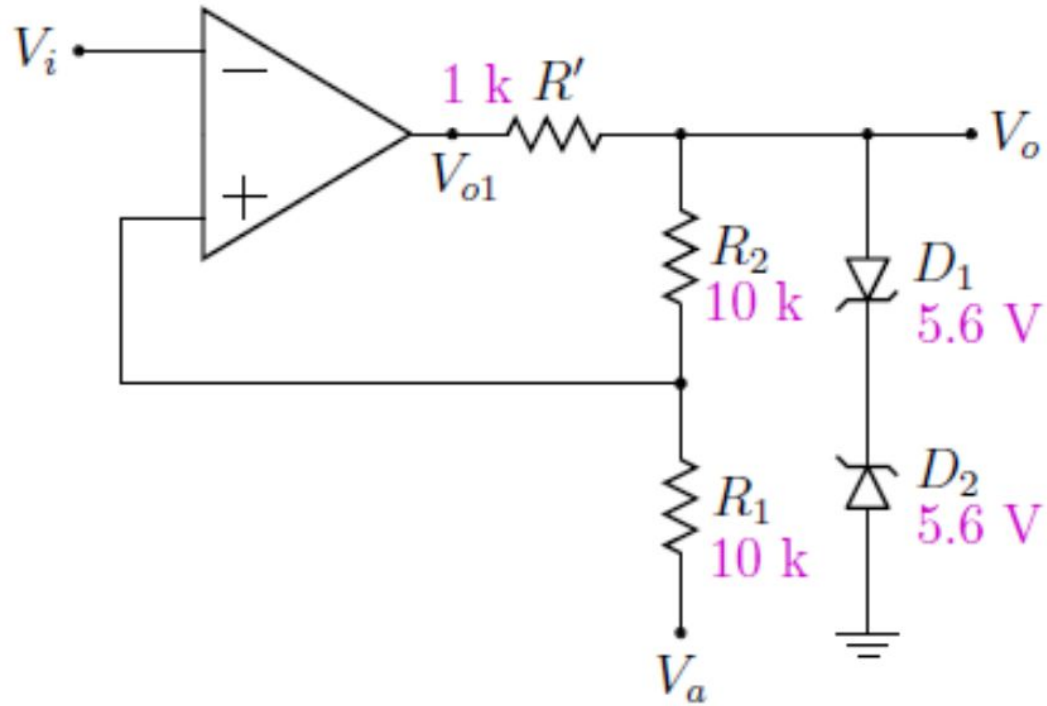

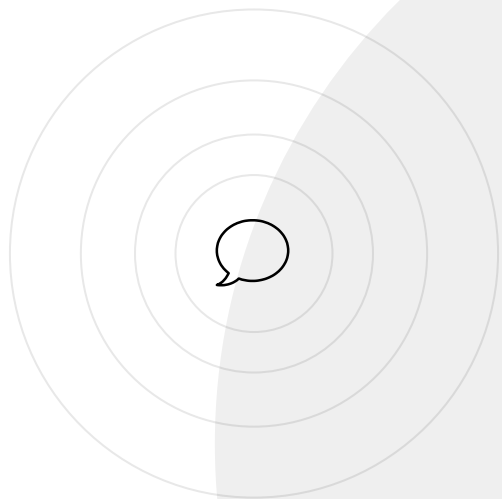

Thank You!

You can contact us at

Yogesh Mahajan

y.mahajan456@gmail.com

Shashank OV

shashankov@iitb.ac.in

Modified Nodal Analysis

$$\begin{bmatrix} A_{rG}GA_{rG}^\top & A_{rT} \\ DA_{rT}^\top & C \end{bmatrix} \begin{bmatrix} v_n \\ i_T \end{bmatrix} = \begin{bmatrix} -A_{rJ}i_J \\ s_T \end{bmatrix} \quad (2.25)$$

For an electrical network having conductances, current sources and voltage sources, MNA equations can be written as

$$\begin{bmatrix} A_{rG}\mathbf{G}A_{rG}^\top & A_{rE} \\ A_{rE}^\top & \mathbf{0} \end{bmatrix} \begin{bmatrix} v_n \\ i_E \end{bmatrix} = \begin{bmatrix} -A_{rJ}i_J \\ v_E \end{bmatrix} \quad (2.26)$$

Reference:

Application of the fast nonlinear DC Analyzer to Min Cost Flow and Single Source Shortest Path Problems – Gaurav trivedi, H. Narayana, S. B. Patkar
Chapter 2