

VHDL Tutorial

OV Shashank

Yogesh Mahajan

Our Assumptions

- Basic (OO)Programming in C/C++/Python
- Basics of Digital Electronics
- GHDL Installation
 - 10.107.2.210/BrC-2018/Installation%20Files/EE4%20_%20EE5/VHDL/
- VHDL Files downloaded
 - 10.107.2.210/BrC-2018/Tutorials/VHDL/

Where might this be useful?

- Courses
 - EE616: Electronic Systems Design
 - EE668 and 671: Systems and VLSI Design
 - EE705: VLSI Design Lab
 - EE709: Testing and Verification of VLSI Circuits
 - EE739: Processor Design
 - EE748: Advanced Topics in Computer Architecture
- Research work involving Design of Systems or FPGAs/CPLD Systems
- As a TA or RA in the WEL Lab or for Undergraduate Courses

Objectives: Not a formal lesson

- What's an HDL?
- What are some HDLs?
- How to get started with VHDL?
 - Designs and Testbenches
- How simulate VHDL?
- Example Codes: Base for the Future

HDL:

Hardware Description Language


And not High-Density Lipo-Protein

Some HDLs:

- VHDL: VHSIC HDL
 - Very High Speed Integrated Circuit
 - Strongly Typed and verbose like C/C++
 - Syntax: Somewhat closer to Python
- Verilog
 - Loose in terms of strictness like Python
 - Syntax similar to C/C++


Moving to Examples

Full Adder

 


Concurrent
Assignments

Drivers

 

Testbench

 


The std_logic type

- 'U': uninitialized. This signal hasn't been set yet.
- 'X': unknown. Impossible to determine this value/result.
- '0': logic 0
- '1': logic 1
- 'Z': High Impedance
- 'W': Weak signal, can't tell if it should be 0 or 1.
- 'L': Weak signal that should probably go to 0
- 'H': Weak signal that should probably go to 1
- '-': Don't care.

Pitfall: Latch Generation


Complete if statement

 
```
if_else: process (sel, a, b)
begin
    if sel = '1' then
        f <= a;
    else
        f <= b;
    end if;
end process;
```



Incomplete if statement

 
```
latching_if: process (sel, a)
begin
    if sel = '1' then
        f <= a;
    end if;
end process;
```



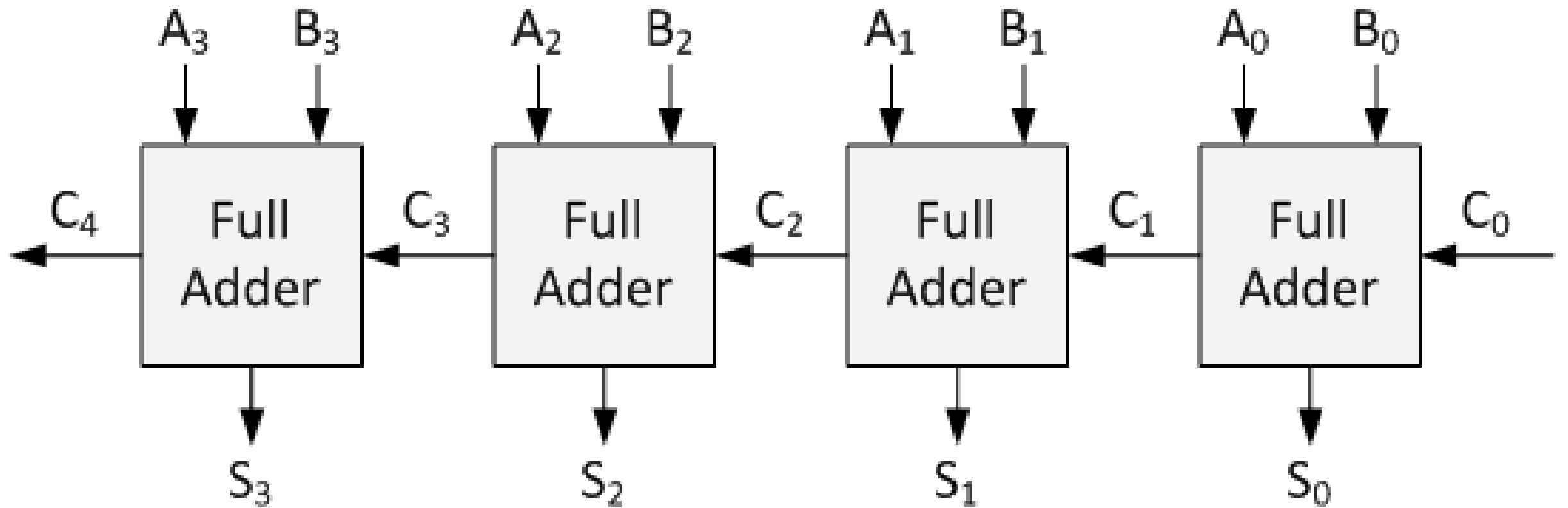




Ripple-Carry Adder

Register

 

Ready - Ready Handshake

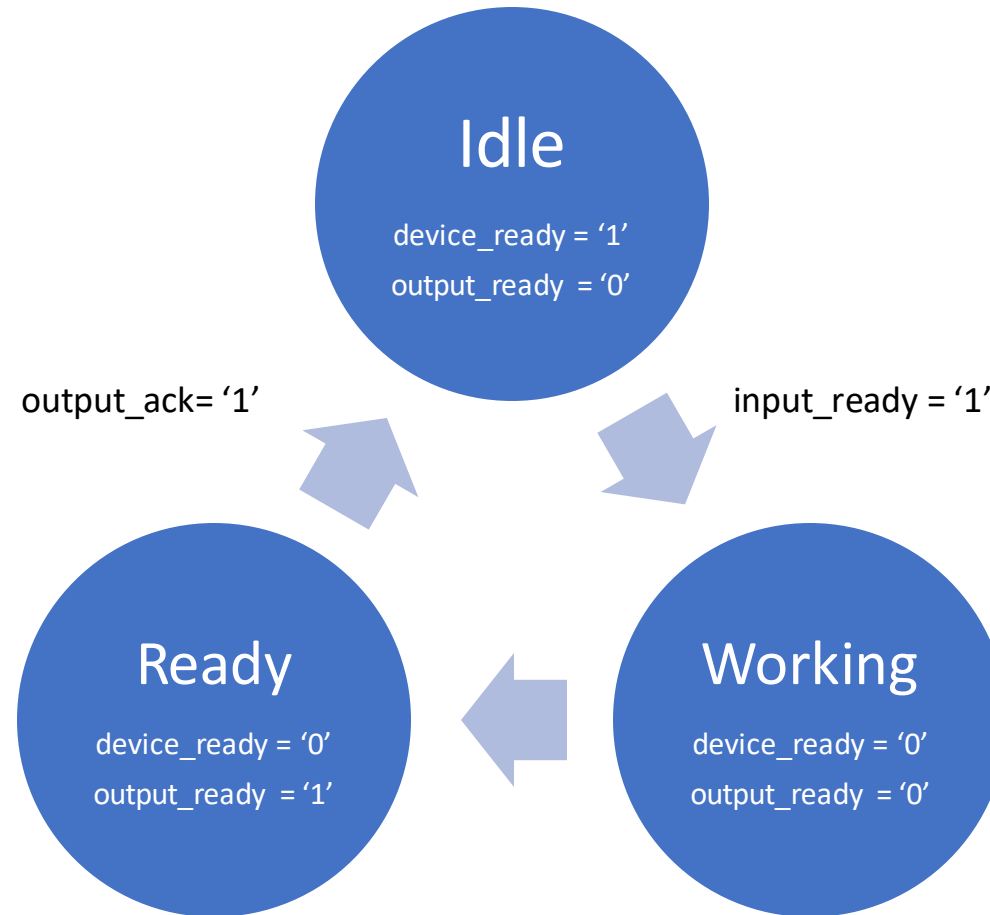

  

Tri-State Buffer

Useful Resources

- GHDL Documentation Provided
- Tutorials
 - https://www.tutorialspoint.com/vlsi_design/vlsi_design_vhdl_introduction.htm
 - <http://www.micc.unifi.it/seidenari/wp-content/uploads/2010/01/vhdl.pdf>
 - https://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html
- Books
 - Digital Design: Principles and Practices, 4th Edition: Wakerly
 - The Designer's Guide to VHDL: Peter Ashenden
- References
 - <https://www.ics.uci.edu/~jmoorkan/vhdlref/>
 - http://web.engr.oregonstate.edu/~traylor/ece474/vhdl_lectures/essential_vhdl_pdfs/
- Debugging
 - Stack Overflow, etc.